

The following equation development should help you to understand how to acquire the output voltage on Slide 17 of Lecture 1. Please note that it could be either a minus or plus sign inside of the parenthesis in the final expression of $V_o(t)$ depending on if $\dot{V}_o(0)$ is positive or negative.

$$\frac{L}{R} \frac{d^2 V_o}{dt^2} + \frac{1}{RC} V_o = 0$$

Conducting Laplace Transform on both sides of equation, we have

$$\frac{L}{R} (s^2 V_o(s) - sV_o(0) - \dot{V}_o(0)) + \frac{1}{RC} V_o(s) = 0$$

$$\frac{L}{R} s^2 V_o(s) + \frac{1}{RC} V_o(s) = \frac{L}{R} (sV_o(0) + \dot{V}_o(0))$$

$$V_o(s) = \frac{\frac{L}{R} sV_o(0)}{\frac{L}{R} s^2 + \frac{1}{RC}} + \frac{\frac{L}{R} \dot{V}_o(0)}{\frac{L}{R} s^2 + \frac{1}{RC}}$$

$$V_o(s) = \frac{sV_o(0)}{s^2 + \frac{1}{LC}} + \frac{\dot{V}_o(0)}{s^2 + \frac{1}{LC}}$$

Conducting inversed Laplace Transform on both sides of the equation above

$$V_o(t) = \underbrace{V_o(0)}_a \cos\left(\frac{1}{\sqrt{LC}} t\right) + \underbrace{\dot{V}_o(0)}_b \sin\left(\frac{1}{\sqrt{LC}} t\right)$$

$$V_o(t) = a \cos\left(\frac{1}{\sqrt{LC}} t\right) + b \sin\left(\frac{1}{\sqrt{LC}} t\right)$$

$$V_o(t) = \sqrt{a^2 + b^2} \left(\frac{a}{\sqrt{a^2 + b^2}} \cos\left(\frac{1}{\sqrt{LC}} t\right) + \frac{b}{\sqrt{a^2 + b^2}} \sin\left(\frac{1}{\sqrt{LC}} t\right) \right)$$

Define $\frac{a}{\sqrt{a^2 + b^2}} = \cos(\varphi)$, and $\frac{b}{\sqrt{a^2 + b^2}} = \sin(\varphi)$

Then we have $V_o(t) = \sqrt{a^2 + b^2} (\cos(\varphi) \cos\left(\frac{1}{\sqrt{LC}} t\right) + \sin(\varphi) \sin\left(\frac{1}{\sqrt{LC}} t\right))$

$$V_o(t) = \underbrace{\sqrt{a^2 + b^2}}_A \cos\left(\frac{1}{\sqrt{LC}} t - \varphi\right)$$

$$V_o(t) = A \cos\left(\frac{1}{\sqrt{LC}} t - \varphi\right)$$